

## ECEN 620

### Homework #3

Due: 10-23-2025, 11:59PM

**Homeworks will not be received after due.**


Instructor: Sam Palermo

- 1. VCO Design and Comparison.** This problem compares the design of a ring and LC-oscillator. Refer to the 665 lab notes posted on the website for help in the simulations.

- a. Ring Oscillator Design.** Shown below is a 3-stage ring oscillator that employs a replica-bias scheme to ensure a constant swing over frequency tuning. Design this circuit at the transistor-level to meet the following specifications:

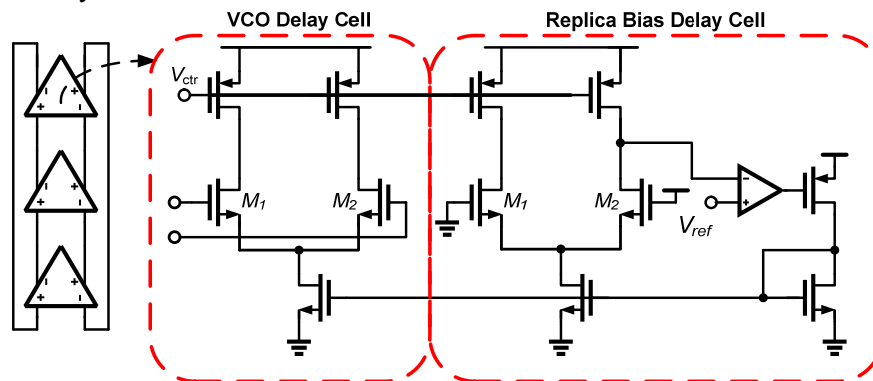- i. 3.125GHz nominal operating frequency
- ii. Phase Noise < -90dBc/Hz @1MHz offset
- iii. Minimum Tuning Range = 1.5GHz to 3.5GHz

You are free to use whatever voltage swing you would like for the ring oscillator. Reasonable swing values are  $0.3-0.5 \cdot V_{DD}$  single-ended peak-to-peak (differential amplitude). Note, there is only one replica bias delay cell that is shared to provide the tail current gate bias voltage for all the 3 VCO delay cells.



3-stage differential ring oscillator.

- b. LC Oscillator Design.** Design an LC-oscillator at the transistor-level to meet the following specifications:

- i. 3.125GHz nominal operating frequency
- ii. Phase Noise < -90dBc/Hz @1MHz offset. Note, this should be easier for this design, relative to the previous ring oscillator.
- iii. Minimum Tuning Range = 2.8GHz to 3.5GHz

You are free to use whatever topology you would like. If you do not have a design kit inductor model, then use a maximum  $Q=5$  and model this with a series resistor. If you do have access to a design kit inductor, then using a  $Q>5$  is fine.

- c. ISF Simulations.** Obtain the impulse sensitivity function for both the designed ring and LC oscillators by following the procedure outlined in the “VCO ISF Simulation” notes on the website. Place a single noise current source on one of the oscillators’ output (single-ended) nodes to obtain the ISF.

- i. Use a minimum of 100 phase points to construct the ISF function.
- ii. Normalize the LC oscillator ISF for an absolute peak of 1, as the notes describe.
- iii. Use the same LC oscillator normalization factor to scale the ring oscillator ISF.
- iv. Plot both of the normalized LC and ring oscillator ISFs on a single plot and comment on the differences.

- d. **Oscillator Comparison.** Make a summary table that compares the two oscillators. One row of the table should be the following figure-of-merit (FOM) which normalizes phase noise performance with oscillator power

$$\text{FOM} = \left( \frac{f_0}{f_m} \right)^2 \frac{1}{L(f_m)P_{avg}},$$

where  $f_0$  is the 3.125GHz oscillation frequency,  $f_m$  is the 1MHz offset,  $L(f_m)$  is the phase noise, and  $P_{avg}$  is the oscillator average power consumption.

2. **Divider Design.** Design a dual-modulus divider which realizes a divide-by-31/32 function and can operate at a maximum 3.5GHz input frequency. Simulate the divider with both the designed ring and LC-oscillators from Problem 1.