

ECEN620 HW2

Evan Hsu 337001800

1. Phase Detector Characterization.

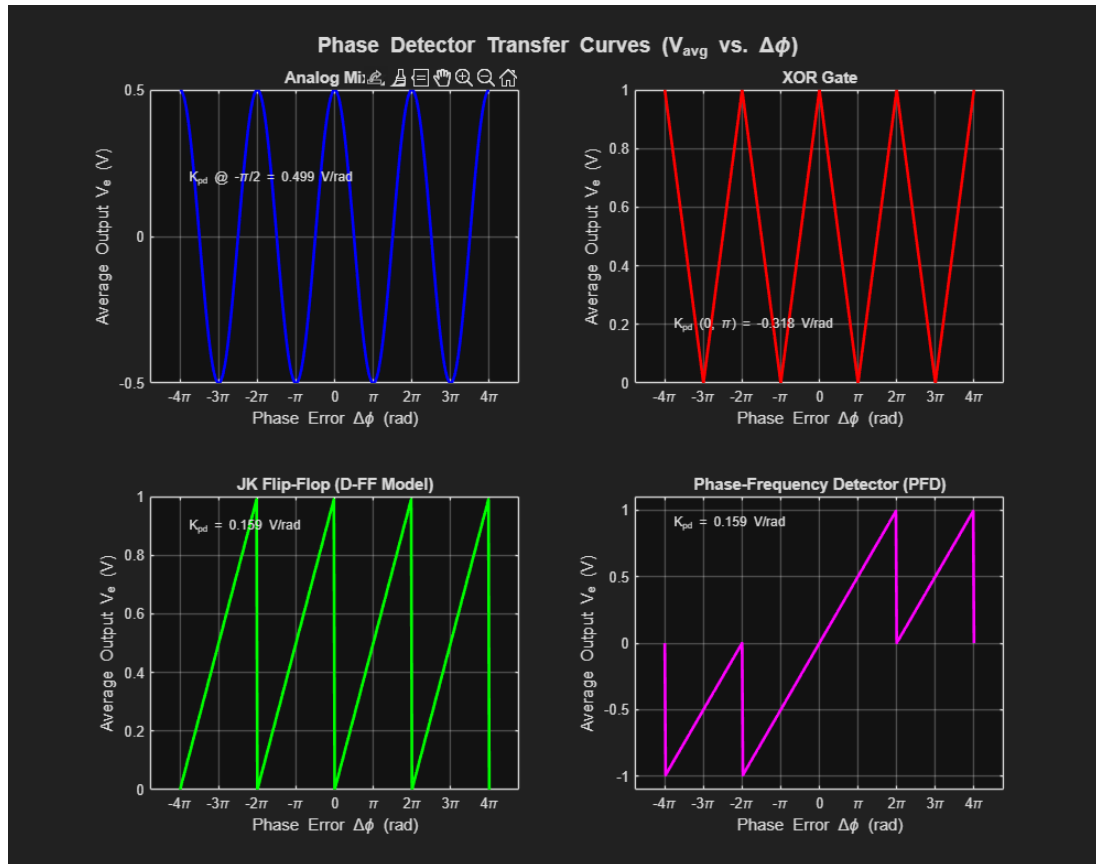


Figure 1. Transfer Curves (avg(V_e) vs Φ_e)

--- Simulation Results: avg(v_e) ---				
Phase Detector	$f_{fb} = 0.50x f_{ref}$	$f_{fb} = 0.75x f_{ref}$	$f_{fb} = 1.50x f_{ref}$	$f_{fb} = 2.00x f_{ref}$
Analog Mixer	+0.0000 V	+0.0000 V	+0.0000 V	+0.0001 V
XOR Gate	+0.4994 V	+0.4995 V	+0.4991 V	+0.4989 V
JK Flip-Flop	+0.5000 V	+0.5000 V	+0.5000 V	+0.0000 V
PFD	+0.5000 V	+0.5012 V	-0.4975 V	-0.5000 V

Figure 2. average output with $ffb=0.5, 0.75, 1.5$, and $2f_{ref}$

The simulation values reveal that only the Phase-Frequency Detector (PFD) is truly useful as a frequency detector. The other circuits are poor at this task because

they lack the ability to provide directional information.

2. Phase-Frequency Detector Design.

 


Figure 3. PFD output pulse=182ps>100ps

 


Figure 4. This simulation result with Reset Delay.

3. Charge Pump Design.

 


Figure 5. (3-a) Peak (absolute value) Transient Iout

 


Figure 6. (3-a) Average Iout

 


Figure 7. (3-a)Phase Error

 


Figure 8. (3-b)Peak (absolute value) Transient Iout

 


Figure 9. (3-b)Average lout

 


Figure 10. (3-b)Phase Error

3-c. Implementing feedback biasing in the PLL makes its performance stable and predictable against variations in

the manufacturing Process, supply Voltage, and operating Temperature (PVT). Feedback biasing uses a control loop (an op-amp) to create a self-correcting mechanism that maintains a constant, desired parameter despite PVT variations