

October 28, 2025

## ECEN 620

### Homework #4

Due: 11-4-2025, 11:59PM

**Homeworks will not be received after due.**

Instructor: Sam Palermo

1. Let's consider a second-order digital PLL that utilizes the PI filter from Lecture 9.

$F_{\text{ref}}=156.25\text{MHz}$

$N=16$

$\Delta_t=10\text{ps}$

$(V_{\text{FS}}/2^B)K_{\text{VCO}}=2\pi*5\text{MHz/LSB}$

- Follow the Lecture 9 design procedure and find the loop filter parameters  $\alpha$  and  $\beta$  for  $f_u=5\text{MHz}$  and  $\Phi_m=60^\circ$ .
- Implement a linear macromodel (MATLAB, etc.) for the closed-loop system.
  - Plot the open-loop gain magnitude and phase and find the phase margin.
  - Plot the output phase transfer function (magnitude only) from 10kHz to 1GHz.